

SPHJC63 – Digital Electronics



Er R Sithikraja MSc, ME, UGCNET

Department of Physics

CPA College Bodinayakanur



Lecture 13: Sequential Logic Counters and Registers

Counters

- Introduction: Counters
- Asynchronous (Ripple) Counters
- Asynchronous Counters with MOD number $< 2^n$
- Asynchronous Down Counters
- Cascading Asynchronous Counters

Lecture 13: Sequential Logic Counters and Registers

- Synchronous (Parallel) Counters
- Up/Down Synchronous Counters
- Designing Synchronous Counters
- Decoding A Counter
- Counters with Parallel Load

Lecture 13: Sequential Logic Counters and Registers

Registers

- Introduction: Registers
 - ❖ Simple Registers
 - ❖ Registers with Parallel Load
- Using Registers to implement Sequential Circuits
- Shift Registers
 - ❖ Serial In/Serial Out Shift Registers
 - ❖ Serial In/Parallel Out Shift Registers
 - ❖ Parallel In/Serial Out Shift Registers
 - ❖ Parallel In/Parallel Out Shift Registers



Lecture 13: Sequential Logic Counters and Registers

- Bidirectional Shift Registers
- An Application – Serial Addition
- Shift Register Counters
 - ❖ Ring Counters
 - ❖ Johnson Counters
- Random-Access Memory (RAM)



Introduction: Counters



- Counters are circuits that cycle through a specified number of states.
- Two types of counters:
 - ❖ synchronous (parallel) counters
 - ❖ asynchronous (ripple) counters
- Ripple counters allow some flip-flop outputs to be used as a source of clock for other flip-flops.
- Synchronous counters apply the same clock to all flip-flops.

Asynchronous (Ripple) Counters

- Asynchronous counters: the flip-flops do not change states at exactly the same time as they do not have a common clock pulse.
- Also known as **ripple counters**, as the input clock pulse “ripples” through the counter – cumulative delay is a drawback.
- n flip-flops \rightarrow a MOD (modulus) 2^n counter. (Note: A MOD- x counter cycles through x states.)
- Output of the last flip-flop (MSB) divides the input clock frequency by the MOD number of the counter, hence a counter is also a *frequency divider*.

Asynchronous (Ripple) Counters

  - Example: 2-bit ripple binary counter.
- Output of one flip-flop is connected to the clock input of the next more-significant flip-flop.





Timing diagram

00 → 01 → 10 → 11 → 00 ...


Asynchronous (Ripple) Counters

- Example: 3-bit ripple binary counter.

  



Asynchronous (Ripple) Counters

 - Propagation delays in an asynchronous (ripple-clocked) binary counter.
- If the accumulated delay is greater than the clock pulse, some counter states may be misrepresented!




Asynchronous (Ripple) Counters

  - Example: 4-bit ripple binary counter (negative-edge triggered).



Asyn. Counters with MOD no. $< 2^n$


 
- States may be skipped resulting in a **truncated sequence**.
- Technique: force counter to *recycle before going through all of the states* in the binary sequence.
- Example: Given the following circuit, determine the counting sequence (and hence the modulus no.)



Asyn. Counters with MOD no. $< 2^n$

- Example (cont'd):



All J, K inputs are 1 (HIGH).

  

MOD-6 counter produced by clearing (a MOD-8 binary counter) when count of six (110) occurs.


Asyn. Counters with MOD no. $< 2^n$

  - Example (cont'd): Counting sequence of circuit (in CBA order).




Asyn. Counters with MOD no. < 2ⁿ

 - *Exercise:* How to construct an asynchronous MOD-5 counter? MOD-7 counter? MOD-12 counter?
- *Question:* The following is a MOD-? counter?




Asyn. Counters with MOD no. $< 2^n$

 - Decade counters (or BCD counters) are counters with 10 states (modulus-10) in their sequence. They are commonly used in daily life (e.g.: utility meters, odometers, etc.).
- Design an asynchronous decade counter.




Asyn. Counters with MOD no. $< 2^n$

 - Asynchronous decade/BCD counter (cont'd).




Asynchronous Down Counters

 - So far we are dealing with *up counters*. *Down counters*, on the other hand, count downward from a maximum value to zero, and repeat.
- Example: A 3-bit binary (MOD- 2^3) down counter.




3-bit binary
up counter

 

3-bit binary
down counter

Synchronous (Parallel) Counters

 - **Synchronous (parallel) counters:** the flip-flops are clocked at the same time by a common clock pulse.
- We can design these counters using the sequential logic design process (covered in Lecture #12).
- Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).




Present state		Next state		Flip-flop inputs	
A_1	A_0	A_1^+	A_0^+	TA_1	TA_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

Synchronous (Parallel) Counters

- Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).

Present state		Next state		Flip-flop inputs	
A_1	A_0	A_1^+	A_0^+	TA_1	TA_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1




$TA_1 = A_0$
 $TA_0 = 1$

 

Synchronous (Parallel) Counters

- Example: 3-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J, K inputs).

Present state			Next state			Flip-flop inputs		
A_2	A_1	A_0	A_2^+	A_1^+	A_0^+	TA_2	TA_1	TA_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

   


Synchronous (Parallel) Counters

- Example: 3-bit synchronous binary counter (cont'd).

$$TA_2 = A_1 \cdot A_0$$

$$TA_1 = A_0$$

$$TA_0 = 1$$

 

Synchronous (Parallel) Counters

- Note that in a binary counter, the n^{th} bit (shown underlined) is always complemented whenever

$$\underline{0}11\dots11 \rightarrow \underline{1}00\dots00$$

or $\underline{1}11\dots11 \rightarrow \underline{0}00\dots00$

- Hence, X_n is complemented whenever
 $X_{n-1}X_{n-2} \dots X_1X_0 = 11\dots11$.

- As a result, if T flip-flops are used, then

$$TX_n = X_{n-1} \cdot X_{n-2} \cdot \dots \cdot X_1 \cdot X_0$$

Synchronous (Parallel) Counters


- Example: 4-bit synchronous binary counter.

$$TA_3 = A_2 \cdot A_1 \cdot A_0$$

$$TA_2 = A_1 \cdot A_0$$

$$TA_1 = A_0$$

$$TA_0 = 1$$

 

Synchronous (Parallel) Counters

- Example: Synchronous decade/BCD counter.

<u>Clock pulse</u>	<u>Q_3</u>	<u>Q_2</u>	<u>Q_1</u>	<u>Q_0</u>	
Initially	0	0	0	0	
1	0	0	0	1	$T_0 = 1$
2	0	0	1	0	$T_1 = Q_3'.Q_0$
3	0	0	1	1	
4	0	1	0	0	$T_2 = Q_1.Q_0$
5	0	1	0	1	
6	0	1	1	0	
7	0	1	1	1	$T_3 = Q_2.Q_1.Q_0 + Q_3.Q_0$
8	1	0	0	0	
9	1	0	0	1	
<u>10 (recycle)</u>	<u>0</u>	<u>0</u>	<u>0</u>	<u>0</u>	

Synchronous (Parallel) Counters


- Example: Synchronous decade/BCD counter (cont'd).

$$T_0 = 1$$

$$T_1 = Q_3'.Q_0$$

$$T_2 = Q_1.Q_0$$

$$T_3 = Q_2.Q_1.Q_0 + Q_3.Q_0$$

 

Up/Down Synchronous Counters

- Up/down synchronous counter: a *bidirectional* counter that is capable of counting either up or down.
- An input (control) line Up/\overline{Down} (or simply Up) specifies the direction of counting.
 - ❖ $Up/\overline{Down} = 1 \rightarrow$ Count upward
 - ❖ $Up/\overline{Down} = 0 \rightarrow$ Count downward

Up/Down Synchronous Counters

- Example: A 3-bit up/down synchronous binary counter.

Clock pulse	Up	Q_2	Q_1	Q_0	Down
0	→	0	0	0	—
1	→	0	0	1	—
2	→	0	1	0	—
3	→	0	1	1	—
4	→	1	0	0	—
5	→	1	0	1	—
6	→	1	1	0	—
7	→	—	—	—	—

$$TQ_0 = 1$$

$$TQ_1 = (Q_0 \cdot Up) + (Q_0' \cdot Up')$$

$$TQ_2 = (Q_0 \cdot Q_1 \cdot Up) + (Q_0' \cdot Q_1' \cdot Up')$$

Up counter

$$TQ_0 = 1$$

$$TQ_1 = Q_0$$

$$TQ_2 = Q_0 \cdot Q_1$$

Down counter

$$TQ_0 = 1$$

$$TQ_1 = Q_0'$$

$$TQ_2 = Q_0' \cdot Q_1'$$


Up/Down Synchronous Counters

- Example: A 3-bit up/down synchronous binary counter (cont'd).

$$TQ_0 = 1$$


$$TQ_1 = (Q_0 \cdot Up) + (Q_0' \cdot Up')$$
 
$$TQ_2 = (Q_0 \cdot Q_1 \cdot Up) + (Q_0' \cdot Q_1' \cdot Up')$$



Designing Synchronous Counters

 - Covered in Lecture #12.
- Example: A 3-bit Gray code counter (using JK flip-flops).



Present state			Next state			Flip-flop inputs					
Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+	JQ_2	KQ_2	JQ_1	KQ_1	JQ_0	KQ_0
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	1	0	X	1	X	X	0
0	1	0	1	1	0	1	X	X	0	0	X
0	1	1	0	1	0	0	X	X	0	X	1
1	0	0	0	0	0	X	1	0	X	0	X
1	0	1	1	0	0	X	0	0	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	1	0	1	X	0	X	1	X	0

Designing Synchronous Counters

- 3-bit Gray code counter: flip-flop inputs.

		$Q_1 Q_0$	
		00	01
Q_2	0	00	01
	1	X	X
		11	10
		X	X

$JQ_2 = Q_1 \cdot Q_0'$

		$Q_1 Q_0$	
		00	01
Q_2	0	00	01
	1	X	X
		X	X
		X	X

$JQ_1 = Q_2' \cdot Q_0$

		$Q_1 Q_0$	
		00	01
Q_2	0	00	01
	1	1	X
		X	X
		X	X

$JQ_0 = Q_2 \cdot Q_1 + Q_2' \cdot Q_1'$
 $= (Q_2 \oplus Q_1)'$

		$Q_1 Q_0$	
		00	01
Q_2	0	00	01
	1	1	X
		X	X
		X	X

$KQ_2 = Q_1' \cdot Q_0'$

		$Q_1 Q_0$	
		00	01
Q_2	0	00	01
	1	X	X
		X	X
		X	X

$KQ_1 = Q_2 \cdot Q_0$


		$Q_1 Q_0$	
		00	01
Q_2	0	00	01
	1	X	1
		X	X
		X	X

$KQ_0 = Q_2 \cdot Q_1' + Q_2' \cdot Q_1$
 $= Q_2 \oplus Q_1$

Designing Synchronous Counters

- 3-bit Gray code counter: logic diagram.
 
$$\begin{array}{lll} JQ_2 = Q_1 \cdot Q_0' & JQ_1 = Q_2' \cdot Q_0 & JQ_0 = (Q_2 \oplus Q_1)' \\ KQ_2 = Q_1' \cdot Q_0' & KQ_1 = Q_2 \cdot Q_0 & KQ_0 = Q_2 \oplus Q_1 \end{array}$$




Counters with Parallel Load


- Counters could be augmented with parallel load capability for the following purposes:
 - ❖ To start at a different state
 - ❖ To count a different sequence
 - ❖ As more sophisticated register with increment/decrement functionality.

Counters with Parallel Load

 
- Different ways of getting a MOD-6 counter:




(a) Binary states 0,1,2,3,4,5.

 

(b) Binary states 0,1,2,3,4,5.

 

(c) Binary states 10,11,12,13,14,15.

 


(d) Binary states 3,4,5,6,7,8.

Counters with Parallel Load

- 4-bit counter with parallel load.

Clear	CP	Load	Count	Function
0	X	X	X	Clear to 0
1	X	0	0	No change
1	↑	1	X	Load inputs
1	↑	0	1	Next state

 


Introduction: Registers

- An *n-bit register* has a group of n flip-flops and some logic gates and is capable of storing n bits of information.
- The flip-flops store the information while the gates control when and how new information is transferred into the register.
- Some functions of register:
 - ❖ retrieve data from register
 - ❖ store/load new data into register (serial or parallel)
 - ❖ shift the data within register (left or right)

Registers With Parallel Load


- Instead of loading the register at every clock pulse, we may want to control when to load.
- *Loading* a register: transfer new information into the register. Requires a *load* control input.
- *Parallel loading*: all bits are loaded simultaneously.

Registers With Parallel Load

 

Using Registers to implement Sequential Circuits

 - A sequential circuit may consist of a *register* (memory) and a *combinational circuit*.



- The external inputs and present states of the register determine the next states of the register and the external outputs, through the combinational circuit.
- The combinational circuit may be implemented by any of the methods covered in *MSI components* and *Programmable Logic Devices*.

Using Registers to implement Sequential Circuits


- Example 1:

$$A_1^+ = \sum m(4,6) = A_1 \cdot x'$$

$$A_2^+ = \sum m(1,2,5,6) = A_2 \cdot x' + A_2' \cdot x = A_2 \oplus x$$

$$y = \sum m(3,7) = A_2 \cdot x$$

Present state		Input x	Next State		Output y
A_1	A_2		A_1^+	A_2^+	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	0	0	1

 


Using Registers to implement Sequential Circuits

- Example 2: Repeat example 1, but use a ROM.

Address			Outputs		
1	2	3	1	2	3
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	0	0	1

ROM truth table

 


Shift Registers


- Another function of a register, besides storage, is to provide for *data movements*.
- Each *stage* (flip-flop) in a shift register represents one bit of storage, and the shifting capability of a register permits the movement of data from stage to stage within the register, or into or out of the register upon application of clock pulses.

Shift Registers

 
- Basic data movement in shift registers (four bits are used for illustration).




(a) Serial in/shift right/serial out

 


(b) Serial in/shift left/serial out

 


(c) Parallel in/serial out

 


(d) Serial in/parallel out

 

(e) Parallel in / parallel out

 


(f) Rotate right

 

 (g) Rotate left


Serial In/Serial Out Shift Registers

- Accepts data serially – one bit at a time – and also produces output serially.



Serial In/Serial Out Shift Registers

 - Application: Serial transfer of data from one register to another.





Serial In/Serial Out Shift Registers

- Serial-transfer example.

Timing Pulse	Shift register A	Shift register B	Serial output of B
Initial value	1 0 1 1	0 0 1 0	0
After T_1	1 1 0 1	1 0 0 1	1
After T_2	1 1 1 0	1 1 0 0	0
After T_3	0 1 1 1	0 1 1 0	0
After T_4	1 0 1 1	1 0 1 1	1


Serial In/Parallel Out Shift Registers

  - Accepts data serially.
- Outputs of all stages are available simultaneously.




Parallel In/Serial Out Shift Registers

 - Bits are entered simultaneously, but output is serial.



Parallel In/Serial Out Shift Registers

 - Bits are entered simultaneously, but output is serial.



Logic symbol



End of segment